

**PHYSICS**

1. Magnetic field due to one of the sheet

$$B = \frac{\mu_0 K}{2} \text{ Parallel to second sheet}$$


Force on section of width b

$$F = bK\ell \frac{\mu_0 K}{2}$$

Force per unit area

$$P = \frac{F}{\ell b} = \frac{\mu_0 K^2}{2}$$
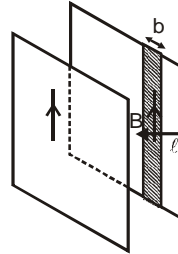
$$P = 4\pi \times 10^{-7} \frac{1}{2\pi}$$



2. Magnetic field due to circular current carrying loop on axis of loop is :

$$B = \frac{\mu_0}{4\pi} \frac{2I\pi R^2}{(R^2 + x^2)^{3/2}}, I = Qf$$


$$B_1 + B_2 = 0$$

$$\frac{Q_1 R^2}{(R^2 + R^2)^{3/2}} + \frac{Q_2 4R^2}{(4R^2 + R^2)^{3/2}} = 0$$

$$\frac{Q_1}{2\sqrt{2}} + \frac{Q_2 4}{5\sqrt{5}} = 0$$

$$\frac{Q_1}{Q_2} = -\frac{8\sqrt{2}}{5\sqrt{5}}$$

- 3.

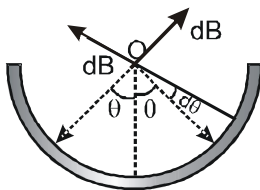

$$dB = \frac{\mu_0 dt}{2\pi R} = \frac{\mu_0 \times \frac{\epsilon}{\ell} (\sigma_0 \cos \theta) R d\theta \times t}{2\pi R}$$

$$B = \int_0^{\pi/2} 2dB \cos \theta = \frac{\mu_0 \sigma_0 \epsilon t}{4\ell}$$


4. No current passes through capacitors in steady state. Assume potential at point '4' to be zero. Then points '1' and '2' are at same potential  $\frac{2V}{3}$ .

Hence  $C_1$  and  $C_2$  can be taken in parallel.

The potential at point 3 is  $\frac{V}{3}$ .

∴ Equivalent circuit of all three capacitors is shown  
Hence potential difference across capacitor  $C_3$  is
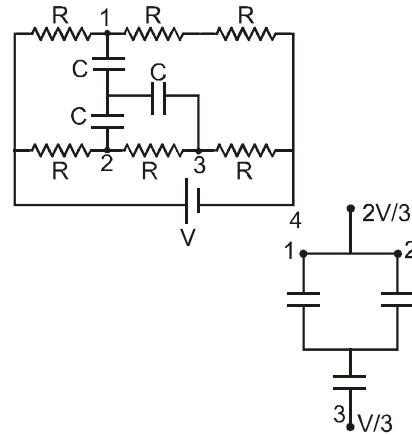
$$= \frac{2C}{2C+C} \times \left( \frac{2V}{3} - \frac{V}{3} \right) = \frac{2V}{9}$$



5.  $P_{B_1 + B_2} = 30 \text{ W}$


$$P_{B_3} = 60 \text{ W}, \quad P_{B_4} = 60 \text{ W}$$

$$P_{B_5} = \frac{(200)^2}{\frac{400^2}{120}} = \frac{120}{4} = 30 \text{ W}$$

$$P_{\text{total}} = 180 \text{ W}$$

6. Since the cell gives out a power of 10W, a current 2A must flow through the cell towards left.  
∴ Power consumed in  $2\Omega$  resistor =  $2^2 \times 2 = 8 \text{ W}$   
Total current flowing in  $1\Omega = 7 \text{ Amp}$ .  
∴ Power consumed by  $1\Omega = 7^2 \times 1 = 49 \text{ W}$

7.

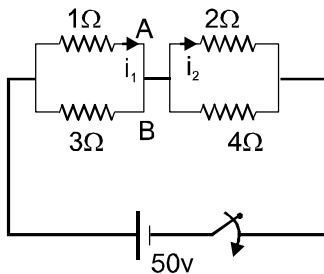


$$R_{\text{eq}} = \frac{3}{4} + \frac{8}{6} = \frac{25}{12} \Rightarrow i_0 = \frac{V}{R_{\text{eq}}} = 24 \text{ Amp.}$$

$$i_1 = \frac{3}{4} \times 24 = 18 \text{ Amp.}, \quad i_2 = \frac{4}{6} \times 24 = 32 \text{ Amp.}$$

Current in the branch AB  
 $\Delta i = 2 \text{ Amp.}$

8.

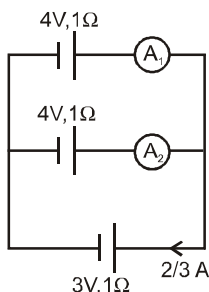

9.  $\tau = RC = \frac{3}{20} \text{ s}$


voltage in capacitor rises to 63% of maximum value.

$$0.63 = (1 - e^{-t/\tau})$$

$$t = 0.15 \text{ s}$$

10. Potential on AB wire is 9V.  
Hence  $\epsilon$  greater than 9v cannot be measured.

11. (i) At  $t > 0$

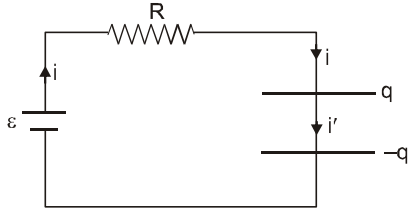

$i'$  = current through dielectric

$$= \frac{q}{C.R.} \quad \dots(i)$$

By K.V.L.  $\epsilon - iR - \frac{q}{C} = 0 \quad \dots(2)$

$$i = i' + \frac{dq}{dt} = \frac{q}{RC} + \frac{dq}{dt} \quad \dots(3)$$

By (2) and  $\epsilon - \left(\frac{q}{RC} + \frac{dq}{dt}\right) R - \frac{q}{C} = 0$

$$\Rightarrow \epsilon C - 2q - RC \frac{dq}{dt} = 0$$

$$\Rightarrow \epsilon C - 2q = RC \frac{dq}{dt} \Rightarrow \int_0^q \frac{dq}{\epsilon C - 2q} = \int_0^t \frac{dt}{RC}$$


$$\Rightarrow -\frac{1}{2} \ln \frac{\epsilon C - 2q}{\epsilon C} = \frac{t}{RC} \Rightarrow q = \frac{\epsilon C}{2} \left(1 - e^{-\frac{2t}{RC}}\right)$$

(ii)  $q_{\max} = \frac{\epsilon C}{2}$  as  $t \rightarrow \infty$


and by (2)  $\epsilon - iR - \frac{\epsilon}{2} = 0$

$$\Rightarrow i = \frac{\epsilon}{2R} \text{ at that time.}$$

- 12.

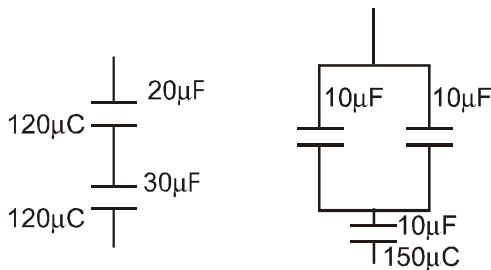

13.

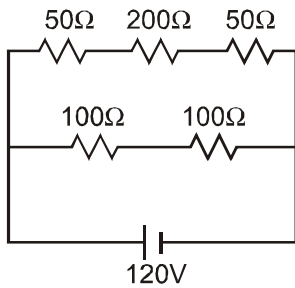

14.

Magnetic field is non zero only in the region between the two solenoids , where  $B = \mu_0 n_2 i_2$

$$\therefore \text{energy stored per unit volume} = \frac{B^2}{2\mu_0} = \frac{\mu_0 n_2^2 i_2^2}{2}$$

The energy per unit length. = energy per unit volume  $\times$  area of cross section where  $B \neq 0$

$$= \frac{\mu_0 n_2^2 i_2^2}{2} [\pi (r_2^2 - r_1^2)] = \frac{\mu_0 n_1^2 i_1^2}{2} [\pi (r_2^2 - r_1^2)], \text{ since } n_1 i_1 = n_2 i_2$$

15.



$$\epsilon_1 = 300 \alpha \quad \dots\dots\dots(i)$$

$$-\epsilon_2 + \epsilon_1 = 100 \alpha \quad \dots\dots\dots(ii)$$

where,  $\alpha$  is the potential gradient

$$\therefore \frac{\epsilon_2}{\epsilon_1} = \frac{2}{3}$$


16.

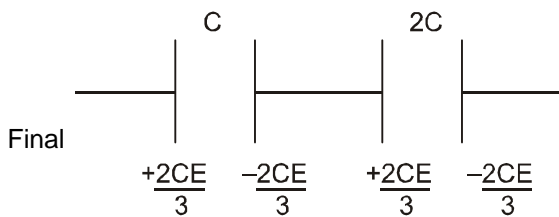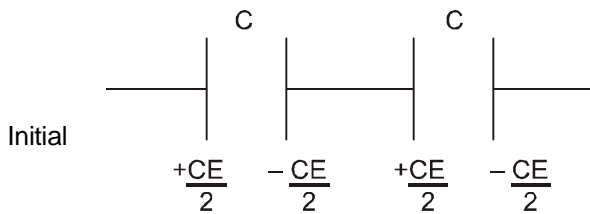

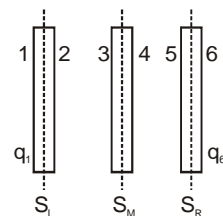17.

Since electric field on plate at surface  $S_L$  is zero, net charge on left side of  $S_L$  is equal to net charge on right side of  $S_L$ . Further net charge between any two dotted surfaces (out of  $S_L$ ,  $S_M$  and  $S_R$ ) is zero from Gauss theorem.

$\therefore$  Charge on left most surface  $q_1$  is equal to charge on right most surface  $q_6$ , that is,  $q_1 = q_6$   
Hence all statements are true.



18. For given condition :

Magnitude of  $B_{\text{solenoid}} = \text{Magnitude of } B_{\text{loop}}$

$$\mu_0 ni = \frac{\mu_0 I}{2R} \quad \text{here } n = \frac{\text{Total no. of turn}}{\text{Total length}} = \frac{1300}{0.65}$$

$$i = \frac{I}{2R} \times \frac{1}{n} = \frac{8 \times 0.65}{2 \times 0.02 \times 1300} = 100 \text{ mA.}$$

For given condition :


Total magnetic field at the centre of loop

$$= |B_{\text{loop}}| + |B_{\text{solenoid}}| \quad \therefore |B_{\text{loop}}| = |B_{\text{solenoid}}|$$


$$= 2|B_{\text{loop}}| = 2 \times \frac{\mu_0 I}{2R}$$

$$= \frac{2 \times 4\pi \times 10^{-7} \times 8}{2 \times 0.02} = 16 \pi \times 10^{-5} \text{ T.}$$

19.

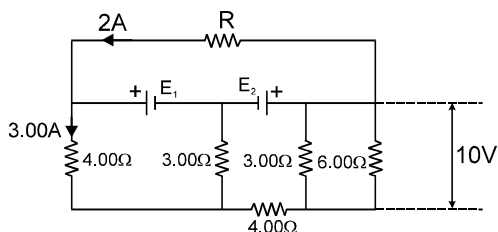

after redrawing the circuit

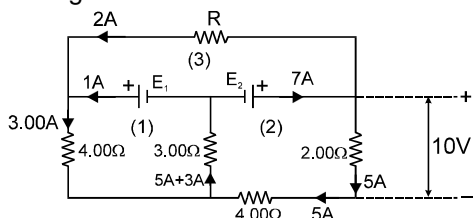

(a)  $I_4 = 5A$

(b) From loop (1) to (1)  
 $-8(3) + E_1 - 4(3) = 0 \Rightarrow E_1 = 36 \text{ volt}$

from loop (2) to (2)  
 $+4(5) + 5(2) - E_2 + 8(3) = 0$   
 $E_2 = 54 \text{ volt}$

(c) from loop (3) to (3)  
 $-2R - E_1 + E_2 = 0$


$$R = \frac{E_2 - E_1}{2} = \frac{54}{2} - 36 = 9 \Omega$$

Ans. (a) 5.00 A (b) 36.0 V, 54.0 V (c) 9.00  $\Omega$

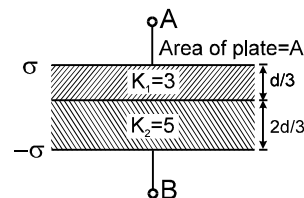20.

$$(i) \frac{e_1}{e_2} = \frac{\epsilon_1 E_1^2}{\epsilon_2 E_2^2} = \frac{k_1 E_1^2}{k_2 E_2^2} = \left(\frac{k_1}{k_2}\right) \left(\frac{k_2}{k_1}\right)^2 = \frac{k_2}{k_1} = \frac{5}{3}$$

$$(ii) \sigma_B = \sigma \left(1 - \frac{1}{k_1}\right) - \sigma \left(1 - \frac{1}{k_2}\right) = \sigma \left(\frac{1}{k_2} - \frac{1}{k_1}\right) = -\frac{2\sigma}{15}$$



21. Potentials are indicated in figure

<b>Resonance</b> Educating for better tomorrow	Corporate Office : CG Tower, A-46 & 52, IPIA, Near City Mall, Jhalawar Road, Kota (Raj.)-324005
	Website : www.resonance.ac.in   E-mail : contact@resonance.ac.in
Toll Free : 1800 200 2244   1800 258 5555   CIN: U80302RJ2007PTC024099	PAGE NO. - 5


$$\text{Current in } 2\Omega = \frac{10 - (-5)}{2} = \frac{15}{2} = 7.5 \text{ A, leftwards}$$

$$\text{Current in } 30\Omega = \frac{10 - (-15)}{30} = \frac{25}{30} = \frac{5}{6} \text{ A, downwards}$$

$$\frac{i_1}{i_2} = 9$$

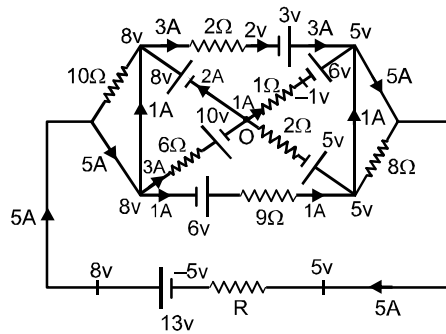
22. Let the junction located at the center of rectangular portion of circuit be at zero potential. Then potentials of many other points can be shown as in figure. Now current can be written in every branch satisfying KCL.

So,  $R = \frac{5 - (-5)}{5} = 2\Omega$  **Ans.**



& Reading of  $A_1 = 0$  **Ans**  
 reading  $A_2 = 5 \text{ A}$  **Ans.**

23.

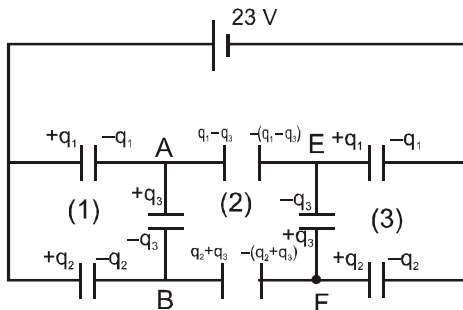

The distribution of charge is shown in figure  $\frac{-q_2}{5} + \frac{q_3}{0.75} + \frac{q_1}{15} = 0$

$$\Rightarrow q_1 - 3q_2 + 20q_3 = 0 \quad \dots\dots\dots(i)$$

$$-\left(\frac{q_2 + q_3}{15}\right) - \frac{q_3}{0.75} + \frac{q_1 - q_3}{5} - \frac{q_3}{0.75} = 0$$

$$\Rightarrow 3q_1 - q_2 - 44q_3 = 0 \quad \dots\dots\dots(ii)$$

$$23 - \frac{q_2}{5} - \left(\frac{q_2 + q_3}{15}\right) - \frac{q_2}{5} = 0$$

$$345 = 7q_2 + q_3 \quad \dots\dots\dots(iii)$$

From eq.(i), (ii), (iii)

$$q_1 = \frac{19 \times 345}{92}, q_2 = \frac{13 \times 345}{92}, q_3 = \frac{345}{92}$$

Potential difference between A and B =  $\frac{q_3}{0.75} = 5V$  **...Ans.**

24. Given circuit can be simplified as dotted part can be replaced as

$$\epsilon_{eq} = \frac{\frac{6}{3} + \frac{0}{6}}{\frac{1}{3} + \frac{1}{6}} = 4V$$




$$\frac{1}{r_{eq}} = \frac{1}{3} + \frac{1}{6} \Rightarrow r_{eq} = 2\Omega$$

then current  $I = \frac{10 - 4}{2 + R} = \frac{6}{2 + R}$

Power in R,  $P = \left(\frac{6}{2 + R}\right)^2 R = \frac{36R}{(2 + R)^2}$ ,

for P to be maximum  $\frac{dP}{dR} = 0$

on solving  $R = 2\Omega$

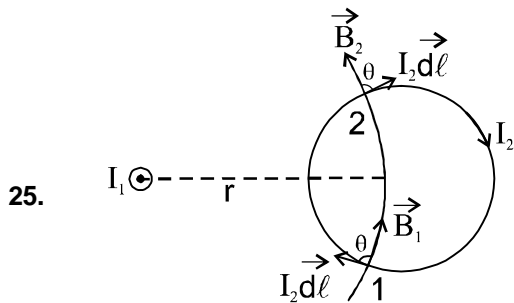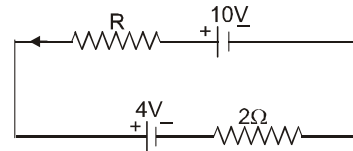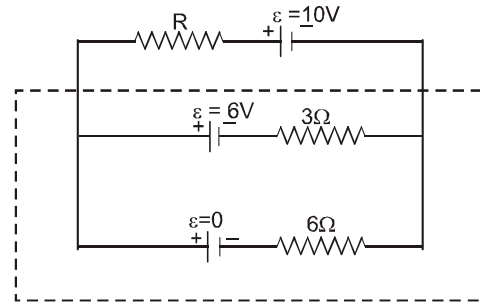

The force on current elements 1 and 2 is equal in magnitude and opposite in direction

$$\Rightarrow F_{net} = 0$$



26.  $B$  at end =  $\frac{1}{2}$   $B$  at interior =  $\frac{1}{2}$   $B$

$$IdL \left(\frac{B}{2}\right) = 2T \sin d\theta$$

$$dL = R(2d\theta)$$

$$I R \cdot 2d\theta \frac{B}{2} = 2T d\theta$$

$$T = \frac{BIR}{2}$$

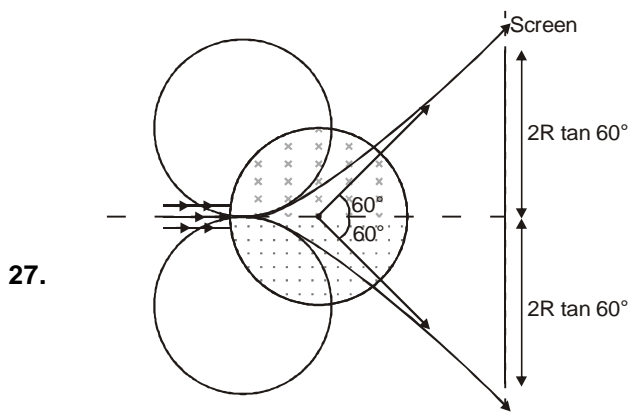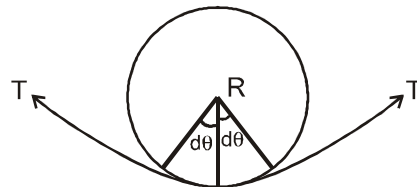

Required  $d = 4R \tan 60^\circ = 4(\sqrt{3})\sqrt{3} = 12$

28.  $R_{AC} = R_{CB} = \frac{2\pi \times 20}{3} \times \frac{3}{\pi} = 40 \Omega$


&  $R_{AD} = R_{BD} = \frac{2\pi \times 20}{3} \times \frac{6}{\pi} = 80 \Omega$

$\Rightarrow$  Balanced W.S.B  $\Rightarrow R_{CD} = \frac{120}{2} = 60 \Omega$

$\varepsilon \times \left( \frac{60}{60+5} \right) = 48 \times$

&  $\varepsilon = x \ell$

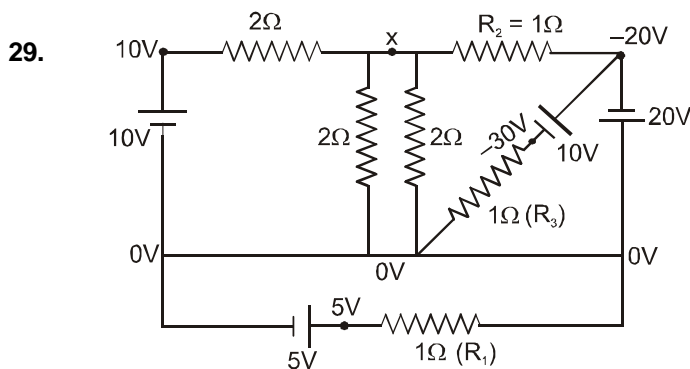$\Rightarrow \ell \times \frac{60}{65} = 48 \Rightarrow \ell = 52 \text{ cm}$



Potential of different points are shown.

(i) current in  $R_1$

$$I_1 = \frac{\Delta V}{R_1} = \frac{5-0}{1} \text{ A} = 5 \text{ A from left to right.}$$

(ii) current in  $R_3$

$$I_3 = \frac{\Delta V}{R_3} = \frac{30}{1} \text{ A} = 30 \text{ A from lower to higher.}$$

(iii) For current in  $R_2$   
using KCL

$$\frac{10-x}{2} + \frac{0-x}{2} + \frac{0-x}{2} + \frac{-20-x}{1} = 0$$

$$\Rightarrow \frac{10}{2} - 20 = \frac{3x}{2} + x \Rightarrow x = -6 \text{ V}$$

$$\therefore I_2 = \frac{20-6}{1} \text{ A} = 14 \text{ A.}$$

30.  $E < 10^6 \Rightarrow \frac{10^3}{d} < 10^6$

$$d > 10^{-3} \text{ m} \Rightarrow C = \frac{k\varepsilon_0 A}{d}$$

$$d = \frac{k\varepsilon_0 A}{C} > 10^{-3}$$

$$A > \frac{10^{-3} \times C}{k\varepsilon_0} \Rightarrow A > \frac{10^{-3} \times 50 \times 10^{-12}}{(6\pi) \times \left( \frac{1}{36\pi} \times 10^{-9} \right)} = 300 \text{ mm}^2$$



31. Applying Energy conservation, initially kinetic energy = 0  
gravitational P.E. = 0 (say) & Magnetic P.E. =  $\mu B$

where,  $\mu$  = magnetic moment of the loop =  $i \cdot \left( \frac{\sqrt{3}a^2}{4} \right)$


Finally when the loop becomes horizontal, Kinetic energy = 0

gravitational P.E. =  $mg \left( \frac{a}{\sqrt{3}} \right)$  (because  $mg$  acts on the centre of mass)

magnetic P.E. = 0

$$\Rightarrow 0 + 0 + \mu B = 0 + \frac{mga}{\sqrt{3}} + 0 \Rightarrow B = \frac{mga}{\sqrt{3}\mu} = \frac{4mg}{3ia}$$

using values,  $B = 400 \text{ mT}$

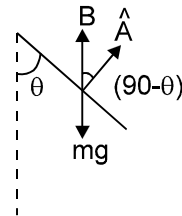

32. Since  $\vec{M} \parallel \vec{B}$

$\therefore$  torque zero.

33. at C direction must be along  $\hat{k}$  direction.

34. The emf is the difference between emf across straight segment OA and OC.

36.  $V_p = x$

$$\frac{3-x}{1} = \frac{x-4}{2} + \frac{x+10}{6}$$

Solve

$$q = 2 \times 4 = 8\mu\text{C}$$

38. The current through the galvanometer is  $\sim \frac{1}{1000}$  of total current, the  $S \ll G$ .

39. Potential difference across galvanometer = Potential difference across S.

$$\Rightarrow i_g \cdot G = (I - i_g) \cdot S$$

$$\Rightarrow 10 \times 10^{-3} \cdot 10 = (1 - 10 \times 10^{-3}) \cdot S \Rightarrow R_s = \frac{10^{-1}}{1-10^{-2}} = \frac{10}{99} \Omega$$


40. At any time  $t$ , the charge on right capacitor be  $q$ . Applying Kirchoff's law

$$\frac{Q_0 - q}{C} = iR + \frac{q}{C} \quad \therefore \frac{Q_0 - 2q}{2CR} = \frac{dq}{dt}$$

integrating and evaluating the constant we get

$$\text{Hence } q = \frac{Q_0}{2} (1 - e^{-\frac{2t}{RC}})$$
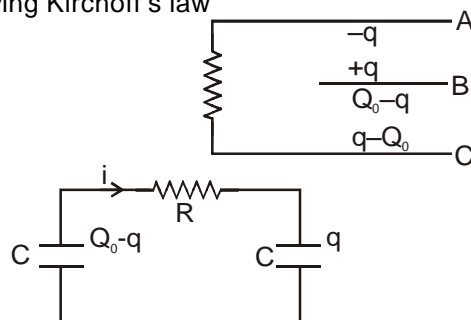
$$\text{or } i = \frac{dq}{dt} = \frac{Q_0}{RC} e^{-\frac{2t}{RC}}$$



41. At steady state charges on both the capacitor will be equal. Hence charge on plate A is  $-Q_0/2$ .

42. Finally the charge on either capacitor is  $Q_0/2$ . Hence heat produced is = initial P.E. - final P.E.

$$= \frac{Q_0^2}{2C} - \frac{(Q_0/2)^2}{2C} - \frac{(Q_0/2)^2}{2C} = \frac{Q_0^2 b}{4S\epsilon_0}$$

43. (A) At constant charge, the electric field within the capacitor remains same when plate separation is changed.

The electric field in capacitor is  $E = \frac{V}{d}$ . Hence at constant potential difference the electric field decreases with increase in  $d$ .

(B)  $U = \frac{1}{2} \frac{Q^2}{C}$ . Hence at constant charge  $U$  increases with decrease in  $C$ .

$U = \frac{1}{2} CV^2$ . Hence at constant potential difference  $U$  decreases with decrease in  $C$ .


(C) Capacitance increases on insertion of dielectric.

(D) As a result of insertion of dielectric the capacitance increases

$U = \frac{1}{2} \frac{Q^2}{C}$ . Hence at constant charge  $U$  decreases with increase in  $C$ .

$U = \frac{1}{2} CV^2$ . Hence at constant potential difference  $U$  increases with increase in  $C$ .

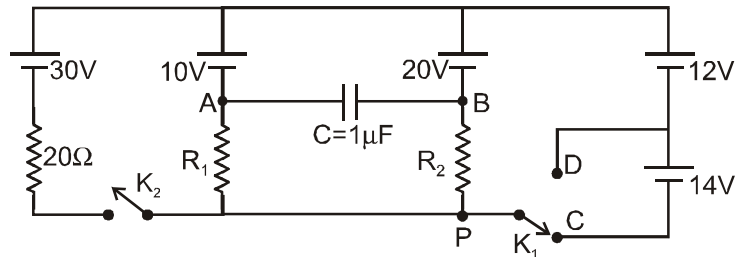44. The state of key  $K_2$  has no effect on current through  $R_1$  and  $R_2$  as well has no effect on charge in the capacitor. Also position of key  $K_1$  has no effect on potential difference between points A and B, that is  $V_A - V_B = 10$  volts under all conditions. Hence charge on capacitor under all cases is  $10\mu C$ .



Assume the potential at point P to be zero,

When Key  $K_1$  is in position C:  $V_A = 16$  Volt and  $V_B = 6$  volts. Hence current in both  $R_1$  and  $R_2$  will flow downwards.

When Key  $K_1$  is in position D:  $V_A = 2$  Volt and  $V_B = -8$  volts. Hence current through  $R_1$  will flow downwards and through  $R_2$  will flow upwards.